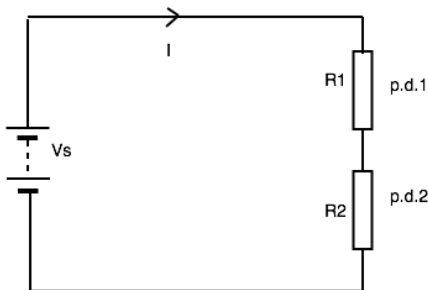


## 5.5 Potential dividers

Look at the following potential divider:



$V_s$  is the supply voltage and p.d.<sub>1</sub> and p.d.<sub>2</sub> are the p.d.s dropped across two resistors  $R_1$  and  $R_2$ .  $I$  is the current flowing. We know that:

$$V_s = p.d._1 + p.d._2$$


and:

$$p.d._1 = IR_1 \text{ and } p.d._2 = IR_2$$

We can see that the supply voltage is divided up between the two resistors depending on their resistance. If one has a bigger resistance than the other, it will get a bigger proportion of the supply voltage. This is why this circuit is an example of a potential divider, because the resistors are dividing up the voltage (or potential).

It is all about ratios. The ratio  $\frac{p.d._1}{p.d._2}$  is equal to the ratio  $\frac{R_1}{R_2}$ .

Lets look at an example:

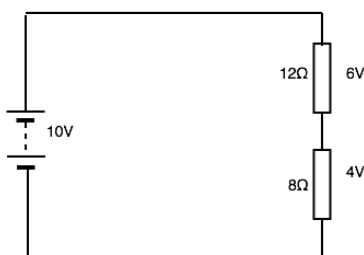


The ratio of  $12\Omega/8\Omega$  is equal to the ratio  $6V/4V$ . Additionally the voltage of the power supply ( $=10V$ ) is equal to the sum of the p.d.s ( $6V + 4V$ ).

(1) ✎ Write down a formula (using  $R_1$ ,  $R_2$  and  $V_s$ ) to find p.d.<sub>1</sub>.

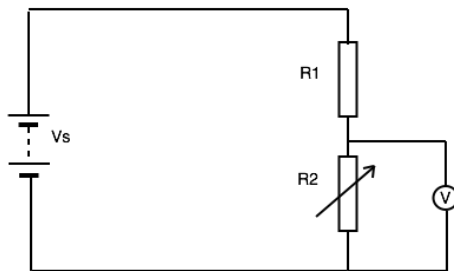(2) ✎ Write down a formula (using  $R_1$ ,  $R_2$  and  $V_s$ ) to find p.d.<sub>2</sub>.


A potential divider circuit is useful when we want to have a variable voltage supply. Look at the following circuit:



$R_2$  is now a variable resistor. This means that the ratio of resistances is variable, and this will affect the p.d. across  $R_2$  (measured with a voltmeter).

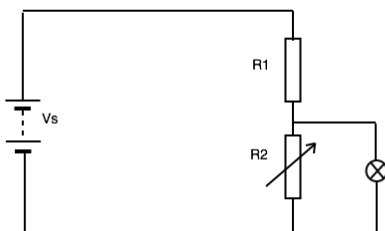
(3) *What will the voltmeter indicate when  $R_2$  is relatively large?*

We can use this circuit to provide a variable voltage to another circuit by connecting across  $R_2$ .



We can adjust the brightness of the lamp using the variable resistor to change the p.d. across the lamp.

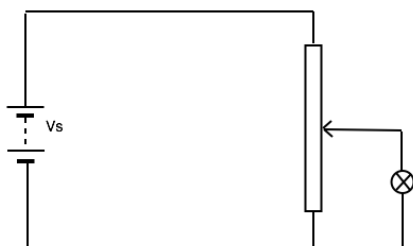
There is a special device designed to be used as a potential divider. This is called a rheostat or potentiometer. It has a sliding contact that changes the ratio of  $R_1$  and  $R_2$ . The following circuit shows such a device:



The total resistance is a constant, but the slide contact means that a variable p.d. can be selected. When the slider is at the top the p.d. will be  $V_s$ . When the slider is at the bottom, the p.d. will be zero.
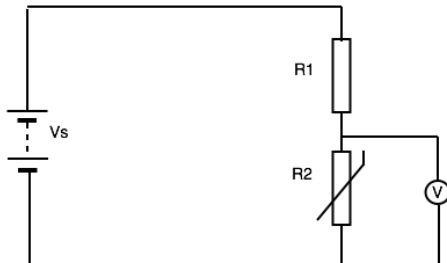
## Sensor circuits

Potential dividers are often used in sensing circuits. A thermistor or LDR can be used in place of  $R_1$  or  $R_2$ . Their resistance changes depending on conditions, hence the p.d. across them. Look at the following example:



Here we have a thermistor in place as  $R_2$ .

(4) *What will happen to the voltmeter reading as the temperature of the thermistor increases?*

(5) *How could you connect the voltmeter in the circuit so that it responds in the opposite sense as the temperature increases?*

(6) *Draw a circuit diagram to show how an LDR could be used as a light level meter. Hint: You may need to adapt your voltmeter!*